

ADDERS AND SUBTRACTORS

AIM:

To develop the source code for adders and subtractors by using VERILOG and obtain the simulation.

ALGORITHM:

Step1: Define the specifications and initialize the design.

Step2 Write the source code in VERILOG


Step3: Check the syntax and debug the errors if found, obtain the synthesis report.

Step4: Verify the output by simulating the source code

BASIC ADDERS & SUBTRACTORS:

HALF ADDER:

LOGIC DIAGRAM:

 

TRUTH TABLE:

A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

VERILOG SOURCE CODE:

Dataflow Modeling:

```
module ha_dataflow(a, b, s, ca);
    input a;
    input b;
    output s;
    output ca;
    assign#2 s=a^b;
    assign#2 ca=a&b;
endmodule
```

Behavioral Modeling:

```
module ha_behv(a, b, s, ca);
    input a;
    input b;
    output s;
    output ca;
    reg s,ca;
    always @(a or b) begin
        s=a^b;
        ca=a&b;
    end
end
```

```
endmodule
```

Structural Modeling:


```
module ha_struct(a, b, s, ca);
  input a;
  input b;
  output s;
  output ca;
  xor
    x1(s,a,b);
  and
    a1(ca,a,b);
endmodule
```

Simulation output:



HALF SUBTRACTOR:

LOGIC DIAGRAM:

 

TRUTH TABLE

A	B	DIFFERENCE	BORROW
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

VERILOG SOURCE CODE:

Dataflow Modeling:

```
module hs_dataflow(a, b, dif, bor);
  input a;
  input b;
  output dif;
  output bor;
  wire abar;
  assign#3 abar=~a;
  assign#3 dif=a^b;
  assign#3 bor=b&abar;
endmodule
```

Behavioral Modeling:

```
module hs_behv(a, b, dif, bor);
```

```

input a;
input b;
output dif;
output bor;
reg dif,bor;
reg abar;
always@(a or b) begin
    abar=~a;
    dif=a^b;
    bor=b&abar;
end
endmodule

```

Structural Modeling:

```


module hs_struct(a, b, dif, bor);
    input a;
    input b;
    output dif;
    output bor;
    wire abar;
    xor
    x1(dif,a,b);
    not
    n1(abar,a);
    and
    a1(bor,abar,b);
endmodule

```



FULL ADDER:

LOGIC DIAGRAM:

 

TRUTH TABLE:

A	B	C	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

VERILOG SOURCE CODE:

Dataflow Modeling:

```

module fulladddataflow(a, b, cin, sum, carry);

```

```

input a;
input b;
input cin;
output sum;
output carry;
assign sum=a^b^cin;
assign carry=(a & b) | (b & cin) | (cin & a);
endmodule

```

Behavioral Modeling:

```

module fuladbehavioral(a, b, c, sum, carry);
input a;
input b;
input c;
output sum;
output carry;
reg sum,carry;
reg t1,t2,t3;
always @ (a or b or c) begin
sum = (a^b)^c;
t1=a & b;
t2=b & c;
t3=a & c;
carry=(t1 | t2) | t3;
end
endmodule

```


Structural Modeling:

```

module fa_struct(a, b, c, sum, carry);
input a;
input b;
input c;
output sum;
output carry;
wire p,q,r,s;
xor
x1(p,a,b),
x2(sum,p,c);
and
a1(q,a,b),
a2(r,b,c),
a3(s,a,c);
or
o1(carry,q,r,s);
endmodule


```

Simulation output:

 

FULL SUBTRACTOR:

LOGIC DIAGRAM:

 

TRUTH TABLE:

A	B	C	DIFFERENCE	BORROW
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

VERILOG SOURCE CODE:

Dataflow Modeling:

```
module fulsubdataflow(a, b, cin, diff, borrow);
    input a;
    input b;
    input cin;
    output diff;
    output borrow;
    wire abar;
    assign abar = ~a;
    assign diff = a^b^cin;
    assign borrow = (abar & b) | (b & cin) | (cin & abar);
endmodule
```

Behavioral Modeling:

```
module fulsubbehavioral(a, b, cin, diff, borrow);
    input a;
    input b;
    input cin;
    output diff;
    output borrow;
    reg t1, t2, t3;
    reg diff, borrow;
    reg abar;
    always @ (a or b or cin) begin
        abar = ~a;
        diff = (a^b)^cin;
        t1 = abar & b;
        t2 = b & cin;
        t3 = cin & abar;
        borrow = (t1 | t2) | t3;
    end
endmodule
```


Structural Modeling:

```

module fs_struct(a, b, c, diff, borrow);
  input a;
  input b;
  input c;
  output diff;
  output borrow;
  wire abar,p,q,r,s;
  not
  n1(abar,a);
  xor
  x1(p,a,b),
  x2(diff,p,c);
  and
  a1(q,abar,b),
  a2(r,abar,c),
  a3(s,a,c);
  or
  o1(borrow,q,r,s);
endmodule


```

Simulation output:

 

FULL ADDER USING TWO HALF ADDERS:

LOGIC DIAGRAM:

 

TRUTH TABLE:

A	B	C	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

VERILOG SOURCE CODE:

Structural Modeling:

```

module fa_2ha(a, b, c, sum, carry);
  input a;
  input b;
  input c;
  output sum;


```

```

output carry;
    wire p,q,r;
    ha_dataflow
    h1(a,b,p,q),
    h2(p,c,sum,r);
    or
    o1(carry,q,r);
endmodule
module ha_dataflow(a, b, s, ca);
input a;
input b;
output s;
output ca;
    assign#2 s=a^b;
    assign#2 ca=a&b;
endmodule


```

Simulation output:

 

FULL SUBTRACTOR USING TWO HALF SUBTRACTORS:

LOGIC DIAGRAM:

 

TRUTH TABLE:

A	B	C	DIFFERENCE	BORROW
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

VERILOG SOURCE CODE:

Structural Modeling:

```

module fs_2hs(a, b, c, diff, borrow);
input a;
input b;
input c;
output diff;

output borrow;
wire p,q,r;

```


```

        hs_dataflow
        h1(a,b,p,q),
        h2(p,c,diff,r);
    or
    o1(borrow,q,r);
endmodule

module hs_dataflow(a, b, dif, bor);
    input a;
    input b;
    output dif;
    output bor;
    wire abar;
    assign#3 abar=~a;
    assign#3 dif=a^b;
    assign#3 bor=b&abar;
endmodule

```

Simulation output

 

Result: