

Design of MUX

Experiment no. 8

Date:

Aim:

To design and implement multiplexer using logic gates.


SOFTWARE REQUIRED: LTspice software

THEORY:

MULTIPLEXER:

Multiplexer does the function of transmitting a large number of information units over a smaller number of channels or lines. A digital multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line. The selection of a particular input line is controlled by a set of selection lines. Normally there are 2^n input lines and n selection lines whose bit combination determines which input is selected.

BLOCK DIAGRAM FOR 4:1 MULTIPLEXER

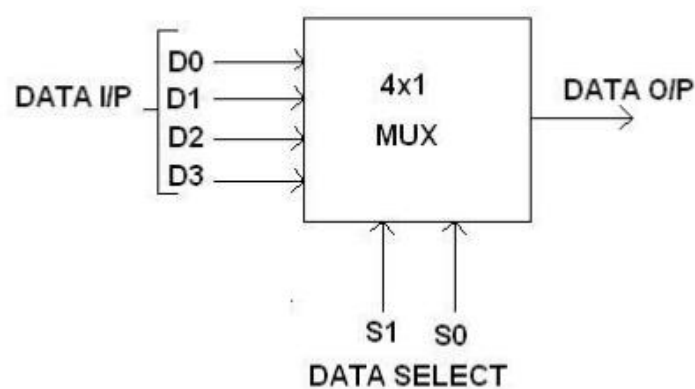


FUNCTION TABLE:

S1	S0	INPUTS Y
0	0	$D0 \rightarrow D0 S1' S0'$
0	1	$D1 \rightarrow D1 S1' S0$
1	0	$D2 \rightarrow D2 S1 S0'$
1	1	$D3 \rightarrow D3 S1 S0$

$$Y = D0 S1' S0' + D1 S1' S0 + D2 S1 S0' + D3 S1 S0$$

CIRCUIT DIAGRAM FOR MULTIPLEXER:

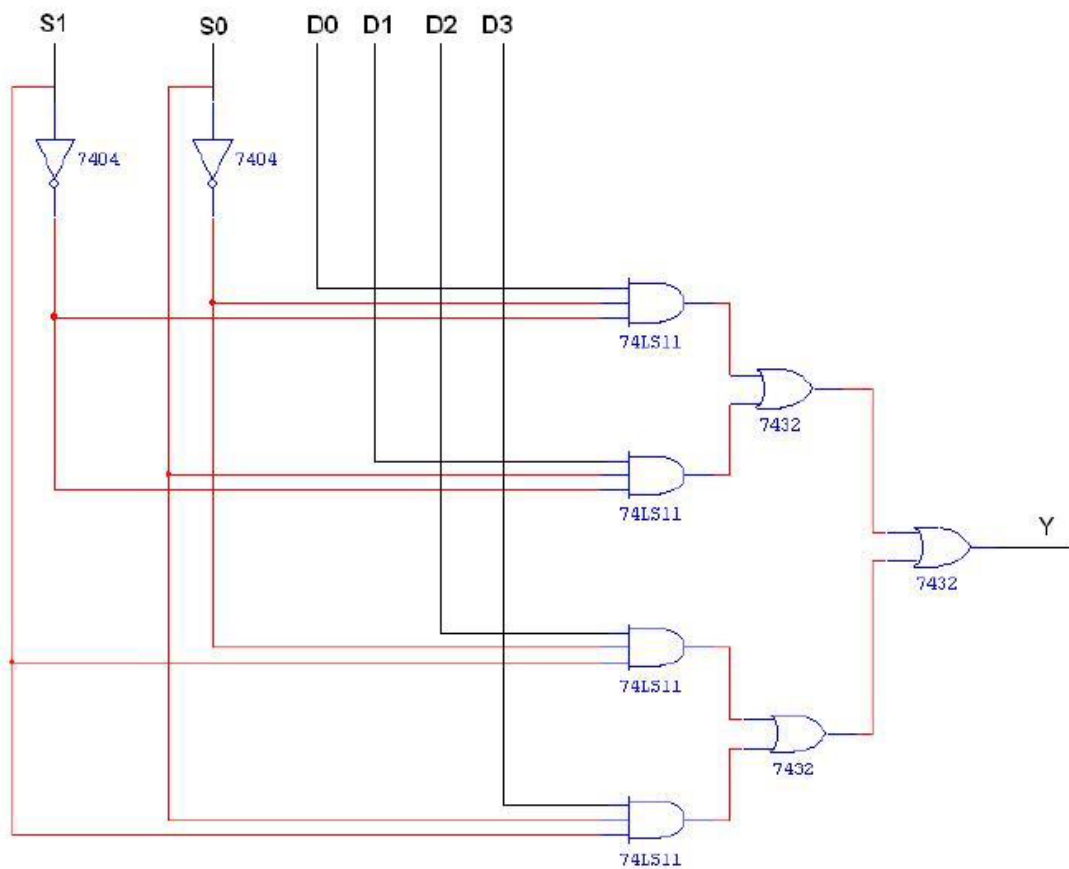


TRUTH TABLE


S1	S0	Y = OUTPUT
0	0	D0
0	1	D1
1	0	D2
1	1	D3

SIMULATION PROCEDURE:

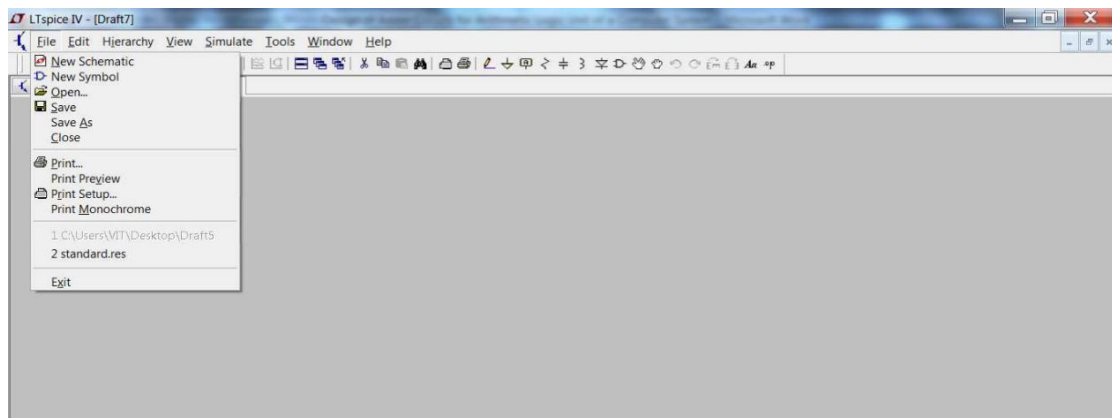
1. Open LTspice. Go to File – New Schematic.



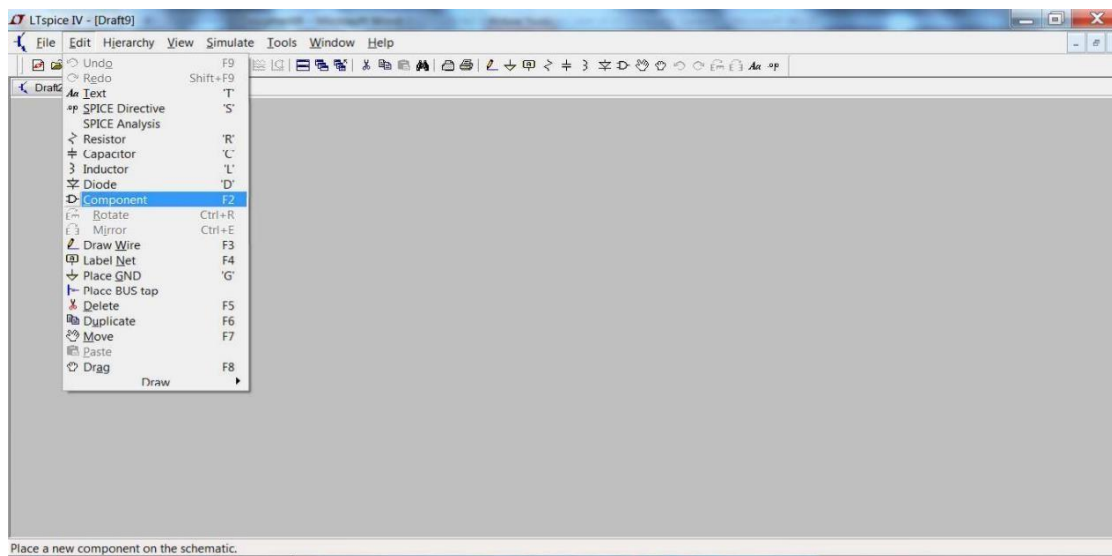
2. On the File Menu, click on Edit – Component.



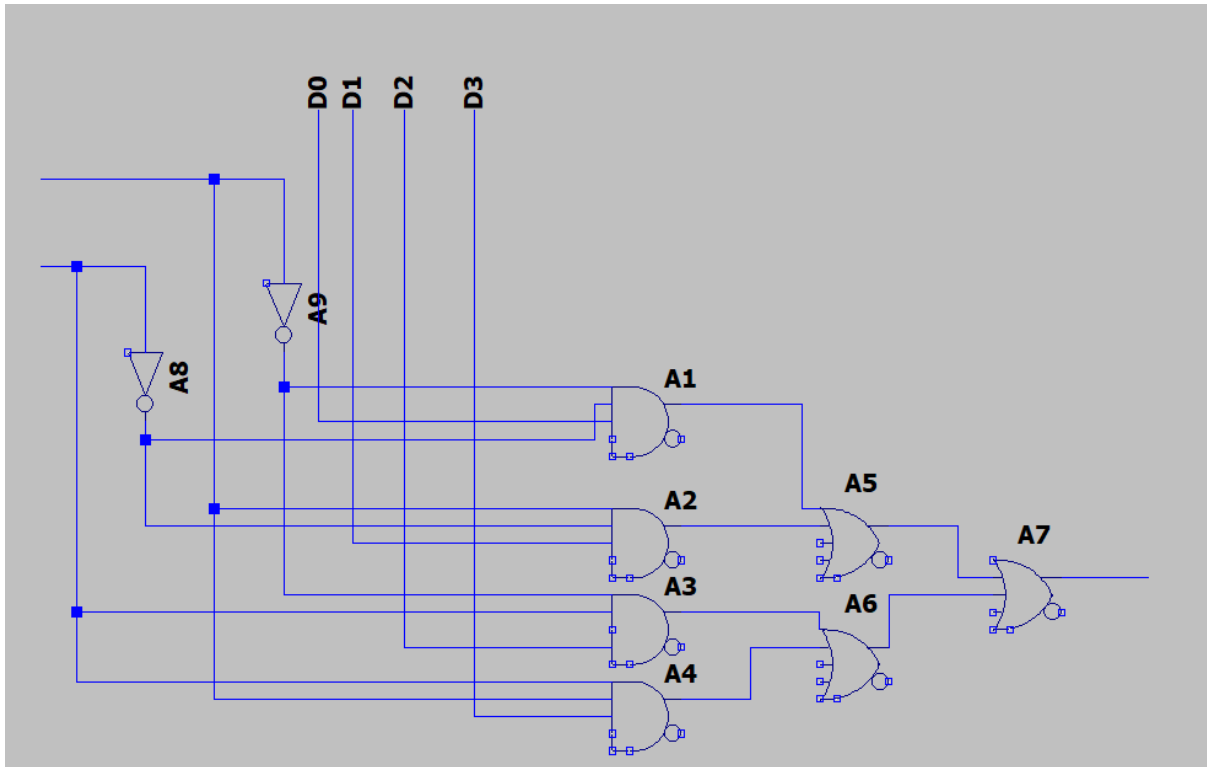3. **a. For Multiplexer:** Place the voltage sources, NOT gate, AND gate, and OR gate on to schematic and make necessary connections as shown in the Figure.




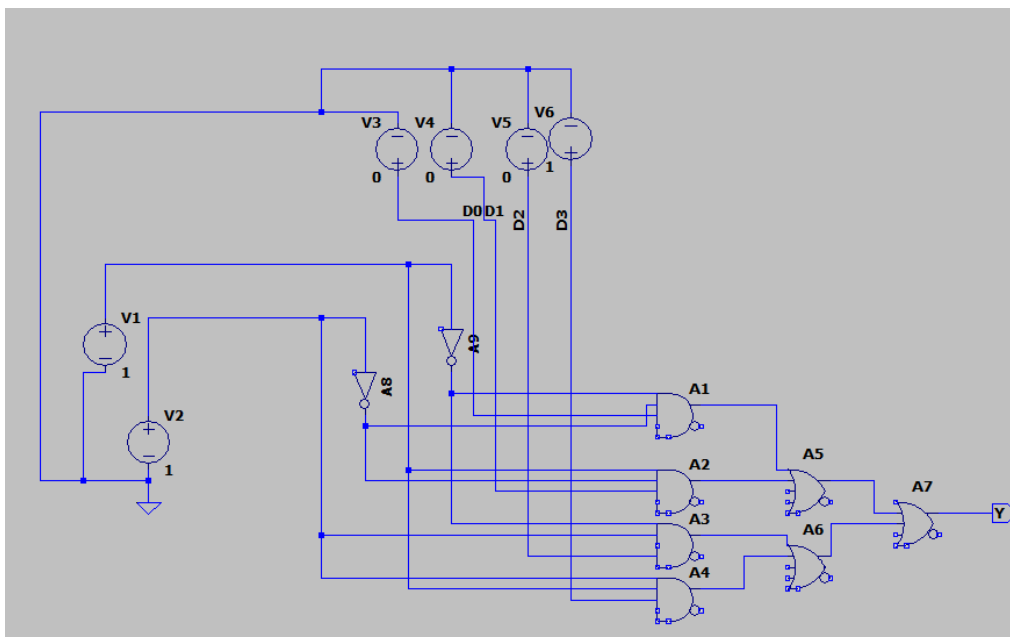- 4.a. Connect the voltage sources as shown Figure for multiplexer.



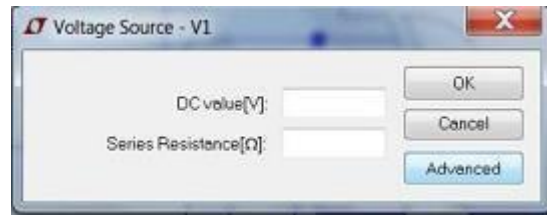
5. For Multiplexer:

Right click on the voltage sources V6 and then Enter DC Value 1 and then click OK option.
Right click on the voltage sources V5 and then Enter DC Value 0 and then click OK option.
Right click on the voltage sources V4 and then Enter DC Value 0 and then click OK option.
Right click on the voltage sources V3 and then Enter DC Value 0 and then click OK option.
Right click on the voltage sources V2 and then Enter DC Value 1 and then click OK option.
Right click on the voltage sources V1 and then Enter DC Value 1 and then click OK option



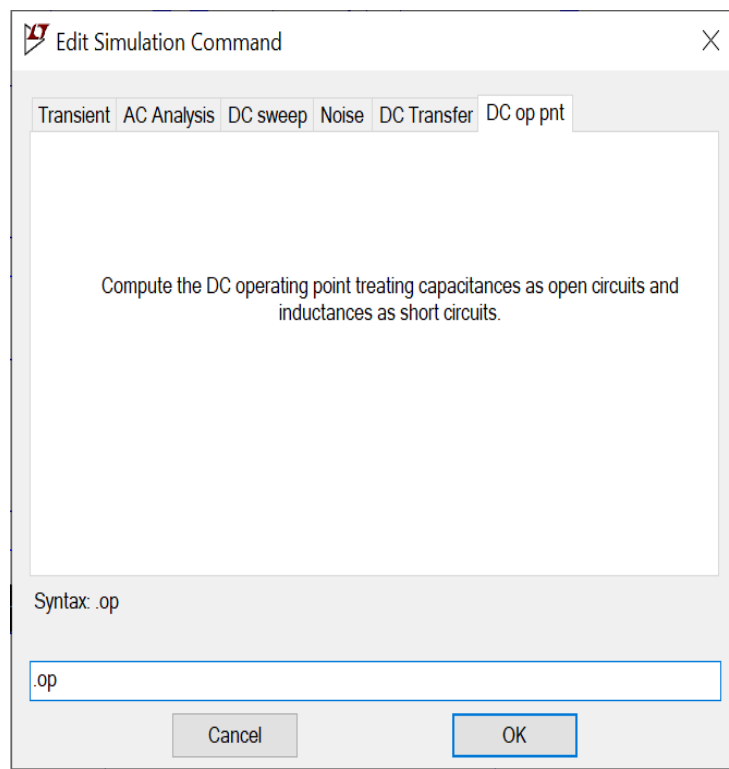6. Go to Edit → SPICE analysis.

For both Decoder and Encoder: Select “DC op pnt” tab and Click “OK” and Press run symbol on menu bar.



Result for Multiplexer:

* C:\Users\gkani\Documents\LTspiceXVII\Draft11.asc		
--- Operating Point ---		
V(n003) :	0	voltage
V(n004) :	0	voltage
V(d0) :	0	voltage
V(n005) :	0	voltage
V(n001) :	1	voltage
V(d1) :	0	voltage
V(n006) :	0	voltage
V(n002) :	1	voltage
V(d2) :	0	voltage
V(n009) :	0	voltage
V(d3) :	1	voltage
V(n010) :	1	voltage
V(n007) :	0	voltage
V(n008) :	1	voltage
V(y) :	1	voltage
I(V4) :	0	device_current
I(V6) :	0	device_current
I(V5) :	0	device_current
I(V3) :	0	device_current
I(V2) :	0	device_current
I(V1) :	0	device_current
I8 (A9) :	-0	device_current
I6 (A9) :	0	device_current
I8 (A8) :	-0	device_current
I6 (A8) :	0	device_current
I8 (A7) :	-0	device_current
I7 (A7) :	0	device_current
I8 (A6) :	-0	device_current

Result

Thus, the multiplexer was implemented and verified using logic gates in LT spice software.