

EXP NO: 01

## VERIFICATION OF LOGIC GATES

### AIM:

To develop the source code for logic gates by using VERILOG and obtain the simulation.

### ALGORITHM:

Step1: Define the specifications and initialize the design.

Step2: Write the source code in VERILOG.

Step3: Check the syntax and debug the errors if found, obtain the synthesis report.

Step4: Verify the output by simulating the source code.


Step5: Write all possible combinations of input using the test bench.

Step6: Obtain the place and route report.

### LOGIC DIAGRAM:

#### AND GATE:

LOGIC DIAGRAM:

 


TRUTH TABLE:

A	B	Y=AB
0	0	0
0	1	0
1	0	0
1	1	1

#### OR GATE:

LOGICDIAGRAM

 


TRUTH TABLE:

A	B	Y=A+B
0	0	0
0	1	1
1	0	1
1	1	1

#### NOT GATE:

LOGIC DIAGRAM:

 


TRUTH TABLE:

A	Y=A'
0	1
1	0

#### NAND GATE:

LOGICDIAGRAM

 

TRUTH TABLE

A	B	Y=(AB)'
0	0	1
0	1	1
1	0	1
1	1	0

#### NOR GATE:

LOGIC DIAGRAM:




TRUTH TABLE:

A	B	Y=(A+B)'
0	0	1
0	1	0
1	0	0
1	1	0

#### XOR GATE:

LOGICDIAGRAM

 


TRUTH TABLE

A	B	Y=A⊕B
0	0	0
0	1	1
1	0	1
1	1	0

**XNOR GATE:**

LOGIC DIAGRAM:

 

TRUTH TABLE:


A	B	$Y = A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

**VERILOG SOURCE CODE:**

```

module logicgates1(a, b, c);
  input a;
  input b;
  OUTPUT: [6:0] c;
    assign c[0]= a & b;
    assign c[1]= a | b;
    assign c[2]= ~(a & b);
    assign c[3]= ~(a | b);
    assign c[4]= a ^ b;
    assign c[5]= ~(a ^ b);
    assign c[6]= ~ a;
end module

```

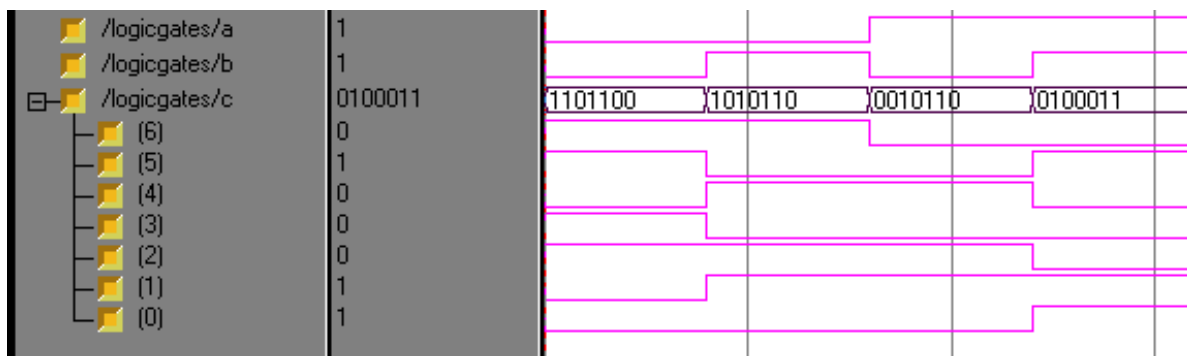**Simulation output:****RESULT:**

Thus, the outputs of Basic Logic Gates are verified by simulating and synthesizing the VERILOG code.